

Electromagnetic Induction

When the magnet moves w.r.t coil the magnetic field \vec{B} created by the magnet at all points of the coil is varied. This variation of \vec{B} sets up an electric current called an induced current in the coil galvanometer circuit.

The existence of such electric currents, in a no generator circuit, is associated with variation of physical quantity called magnetic flux.


$$\vec{B} \left\{ \begin{array}{l} B_0 = 4\pi \times 10^{-7} \times \frac{NI}{R}, \quad N \rightarrow \# \text{ turns} \\ \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad I \rightarrow \text{intensity current} \\ \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad R \rightarrow \text{radius of coil} \\ \text{line of action is along axes of coil} \\ \quad \quad \quad \quad \quad \quad \quad \quad \quad \quad \perp \text{ to plane of coil at its center} \\ \text{Direction is RHR} \end{array} \right.$$

Unit of B is tesla (T)

Laplace's force

$$\vec{F} = I \vec{l} \wedge \vec{B}$$

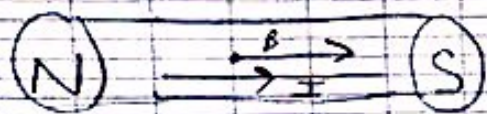\Rightarrow if \vec{I} and \vec{B} $\uparrow\uparrow$ then $\vec{F} = 0$



• We draw \vec{F} at mdpl of wire

$$F_{\text{max}} \left\{ \begin{array}{l} F = I l B \sin(\vec{I}, \vec{B}) \end{array} \right.$$

\perp to plane formed by \vec{I} and \vec{B}

RHR



Magnetic flux

$$\Phi = \vec{B} \cdot \vec{n} \cdot S'$$

\vec{B} : magnetic induction vector of magnetic field

\vec{n} : normal vector \oplus

S' : total area of used coil

• Induction \Rightarrow influence without contact.

$$\Phi = N B S \cos(\vec{B}, \vec{n})$$

Φ = unit = weber (wb)

N = number of turns (m^2)

B = magnitude of \vec{B} (T)

S = area of each coil




$$S' = N \times S$$

ϕ could be +ve -ve or 0
 Depending on $\theta = (\hat{n}, \hat{B})$

① $0 \leq \theta \leq \frac{\pi}{2}$ $\cos \theta > 0$ $\phi > 0$

② $\theta = \frac{\pi}{2}$ $\cos \theta = 0$ $\phi = 0$

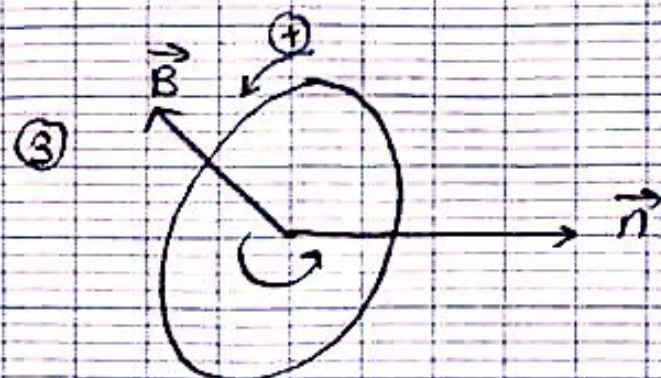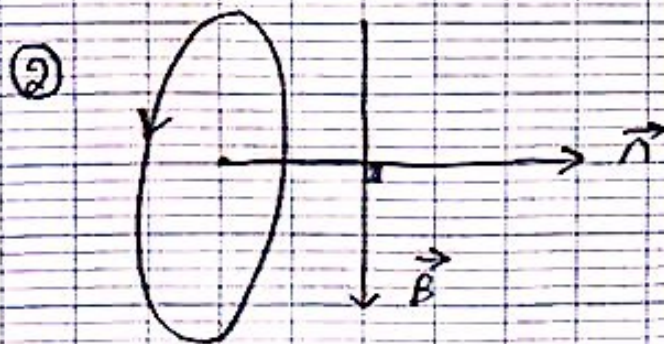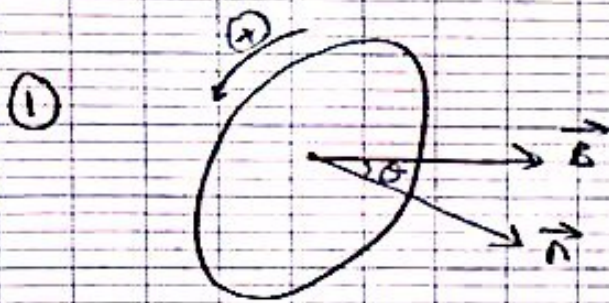③ $\frac{\pi}{2} \leq \theta \leq \pi$ $\cos \theta < 0$ $\phi < 0$



Conclusion :

The phenomenon observed where an electric current traverses a closed circuit crossed by a varying magnetic flux, is called **electromagnetic induction**. The circuit traversed by the induced current is called **induced circuit**. The source of the magnetic field, which is at the origin of the phenomenon of induction, is called **inducing source**.

Note

The establishment of an induced current requires the existence of an **induced electromotive force "e"**. A variation of magnetic flux through a circuit gives rise to an induced e.m.f. "e" whether circuit closed or opened.

- If circuit closed \Rightarrow current
- If circuit opened \Rightarrow no current

Note

The variation of magnetic flux produces an induced voltage whether circuit opened or closed. But when circuit closed it produces induced current such that the current has electromagnetic effect opposes reason producing it.

Farady's Law

$$e = - \frac{d\Phi}{dt}$$

Induced voltage, which is the effect of variation of flux when circuit closed and current pass through.

amp $iR \rightarrow$ resistance of circuit

Lenz's Law

Direction of induced current is such that its electromagnetic effect always oppose the cause producing it.

Note

Resistor $\Rightarrow u = iR$

Generator $\Rightarrow u = E - iR$, E : electromotive force
or if direction opp. of current's dir. then $u = iR - e$


Coil $\Rightarrow u = iR - e$

Exercise


We place a squared coil of $a = 0.05\text{m}$ in a magnetic field with B as a function of time.

Find e induced voltage / electromotive force.

We have 3

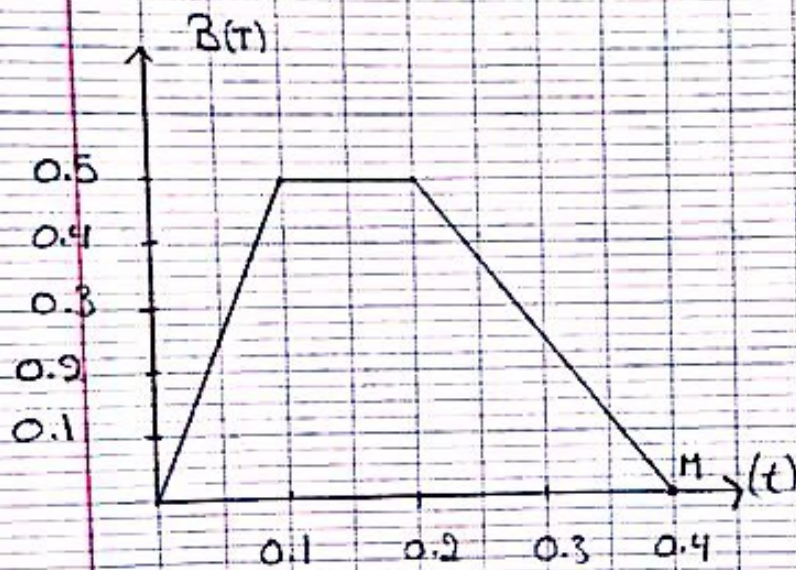

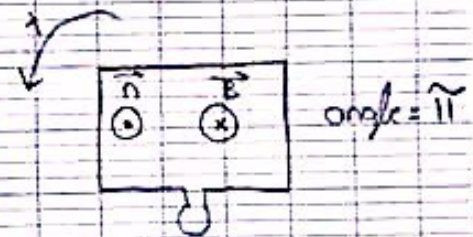- ① Expression of B wrt time
- ② Substitute B in eq of Φ
- ③ Derive Φ to get e
- ④ Deduce sign of i (from e)



• at $0 \leq t \leq 0.1$
 $B = k \times t$ (passing origin)
 $k = \text{slope} = \frac{\Delta y}{\Delta x} = \frac{0.5}{0.1} = 5$
 $B_1 = 5t$

• at $0.1 \leq t \leq 0.2$
 $B_2 = 0.5$ y axis // x axis

• at $0.2 \leq t \leq 0.4$
 $B_3 = k' t + b$ not thru origin (y, ax+b)
 $k' = \frac{-\tan \beta'}{0.2} = -2.5$
 $B_3 = -2.5t + b$



at M
 $0 = -2.5(0.4) + b$
 $b = 1$
 $B_3 = -2.5t + 1$

• $\Phi = BS \cos(\beta, \vec{n})$
 $= -B \cdot a^2$

$\Phi_1 = -1.25t, e_1 = 1.25\text{V}$

$\Phi_2 = 0.125\text{W}, e_2 = 0$

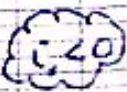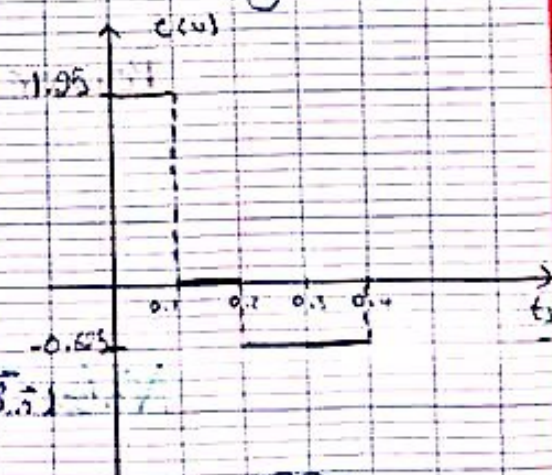$\Phi_3 = 0.625t - 0.25, e_3 = -0.625\text{V}$



Notes from Exercises

$e = \dot{\Phi} \Rightarrow$ stays same since derivative of lin. function of
 $\Phi = kt + \Phi_0$ linear function

if $I_1 \downarrow \vec{B}_1 \downarrow$ flux varies
then to increase \vec{B}_2 fluxes in
same direction of \vec{B}_1 (Lenz's Law) --- RHR

Since $\dot{\Phi} \neq 0 \Rightarrow$ no induced voltage and no induced current

Since oscilloscope has a very high resistance
 \Rightarrow there is a very small current flowing
in circuit which is negligible.

Power

$$P_{\text{total electric power}} = P_{\text{useful or mechanical}} + P_{\text{heat power by joules effect or dissipated}} \quad (\text{Ohm's law generator}) \times i$$

Notes from Exercises

$$1 \text{ turn} = 2\pi \hat{n}$$

$$\text{turns/min} \xrightarrow{\div 60} \text{turns/s}$$

$$(\vec{B}_1, \vec{n}) = \theta = \theta t + \theta_0$$

Electromagnetic Self Induction

$$\Phi = Li^2$$

$$L = 4 \times 10^{-7} \frac{N^2 S}{l} \quad (H) : \text{Henry}$$

The self induced electromotive force

$$\Rightarrow e = - \frac{d\Phi}{dt} = -L \frac{di}{dt}$$

$$U_{\text{coil}} = ri - e \\ = ri + L \frac{di}{dt}$$

During growth phase

when $I \uparrow$ from zero to max; flux varies due to magnetic field with increasing \vec{B} . It's called self flux. But $\Phi = BNS$ $\cos(\vec{B}, \vec{n}) = 0$
since \vec{B} is along axis of coil

$$B = 4 \times 10^{-7} \frac{N}{l} i$$

$$\Rightarrow \Phi = 4 \times 10^{-7} \frac{N^2 S}{l} i \Rightarrow \Phi = Li$$


at $t=0, i=0$

Diff equation

$$E = Ri + L \frac{di}{dt}$$

Solution:
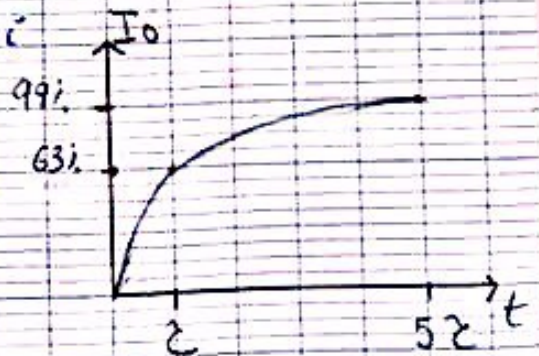
$$i = I_0 \left(1 - e^{-\frac{t}{\tau}} \right)$$



$$\tau = \frac{L}{R}$$

$$\text{and } I = \frac{E}{R}$$

$$\bullet y = Ae^{ax} \Rightarrow y' = A x' e \cdot \left(-\frac{t}{a}\right)' = -\frac{1}{a}$$

• To verify a solution we substitute the given solution in the Diff eq.

$$\text{ex: } i = \frac{E}{R} - \frac{E}{R} e^{-\frac{t}{\tau}}$$

$$E = iR + L \frac{di}{dt}$$

$$\bullet i' = 0 - \frac{E}{R} \left(-\frac{1}{\tau}\right) e^{-\frac{t}{\tau}}$$

$$\bullet i' = \frac{E}{R\tau} e^{-\frac{t}{\tau}}$$

$$E = \left(\frac{E}{R} - \frac{E e^{-\frac{t}{\tau}}}{R}\right) R + L \left(\frac{E}{R\tau} e^{-\frac{t}{\tau}}\right)$$

$$E = E - \frac{E e^{-\frac{t}{\tau}}}{R} + \frac{L}{R} \frac{E}{\tau} e^{-\frac{t}{\tau}}$$

$$E = E - \frac{E e^{-\frac{t}{\tau}}}{R} + E e^{-\frac{t}{\tau}}$$

$$E = E \quad \text{verified.}$$

if the circuit is totally resistive then $i = \frac{e}{R_{\text{total}}}$

i and e always of same sign

if circuit opened no current but still be an electromotive force

Right Hand Rules (RHR)

For Direction of \vec{B}

- ① Thumb toward current. Fingers toward pt. curl 90°
- ② Curl your fingers toward current (solenoid). Your thumb is \vec{B}

For Direction of \vec{F}

Hold the wire. Thumb toward I . Place finger toward B . The third finger is \vec{F} . Knowing that I and B are gun-shaped and \vec{B} and \vec{F} are \perp

Note

Area of 1 disk $\Rightarrow \frac{\pi d^2}{4}$

Exercise

$$\text{Solution } E = iR + L \frac{di}{dt}$$

$$i = A(1 - e^{kt})$$

Determine A and K

$$i = A - Ae^{kt}$$

$$\frac{di}{dt} = -Ake^{kt}$$

$$E = R(A - Ae^{kt}) - LAke^{kt}$$

$$E = RA - RAe^{kt} - LAke^{kt}$$

$$E + 0e^{kt} = RA - Ae^{kt}(R + kL)$$

By identification

$$E = RA \Rightarrow A = \frac{E}{R}$$

$$A(R + kL) = 0$$

$$k = -\frac{R}{L}$$

$$\text{But } \tau = \frac{L}{R}$$

$$\frac{L}{R} = -\frac{1}{k} = \tau$$

$$k = -\frac{1}{\tau}$$

$$i = \frac{E}{R} (1 - e^{-\frac{t}{\tau}})$$

During Decay Phase

Diff Equation

$$0 = iR + L \frac{di}{dt}$$

Solution


$$i = I e^{-\frac{t}{\tau}}$$

at $t = \tau$

$$\Rightarrow i = 37\% I$$

at $t = 5\tau$

$$i = 0$$

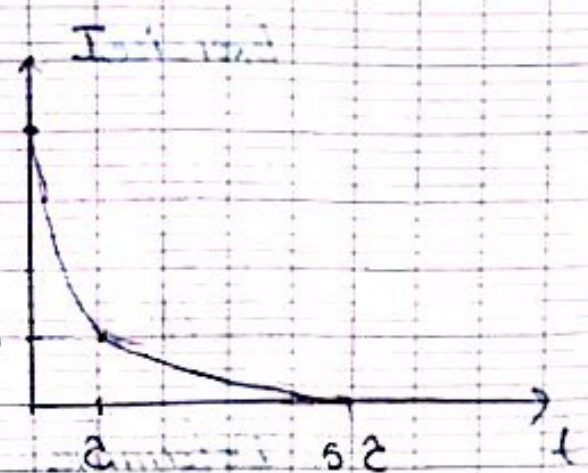

Notes

$$E_{\text{magnetic stored or total}} = \frac{1}{2} Li^2$$

$$E_i = ri^2 + \frac{d}{dt} \left(\frac{1}{2} Li^2 \right)$$

electric energy heat energy electromagnetic energy at certain instant

During Decay phase when self induced emf same direction of current \Rightarrow coil plays role of generator

During Growth phase when self induced emf opp direction (sign) of current \Rightarrow coil receiver or generator opposition

Use graph to Determine τ (time ct)

Tangent Passing Through Origin

$$y = At$$

slope = derivative of function

Given: $i = I(1 - e^{-\frac{t}{\tau}})$

$$\frac{di}{dt} = \frac{I}{\tau} e^{-\frac{t}{\tau}}$$

at $t=0$ $\frac{di}{dt} = \frac{I}{\tau}$

Substitute $M(x, I)$ in $y = \frac{I}{\tau} t$

$$I = \frac{I}{\tau} \tau x$$


$$\frac{x}{\tau} = 1 \Rightarrow x = \tau$$

$$x = OM = \tau$$

Notes


$$\cos' = -\sin$$

$$\sin' = \cos$$

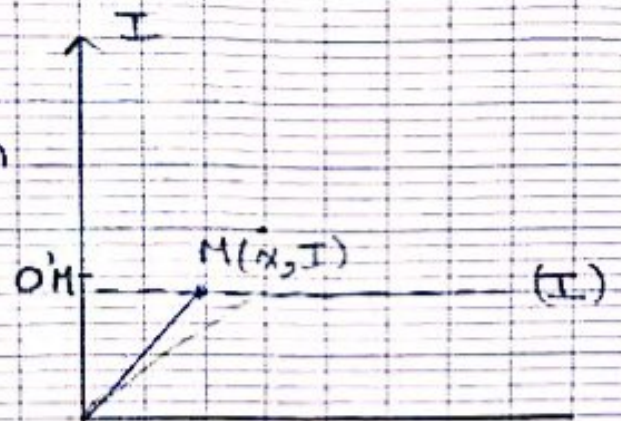

Capacitor

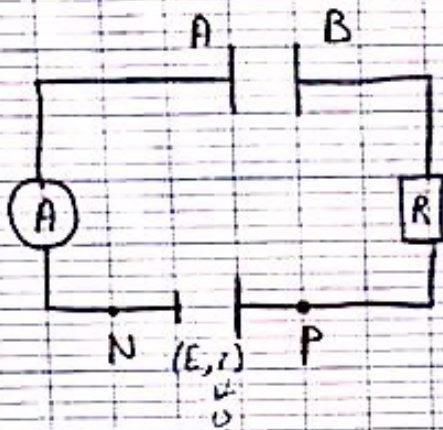It's a system that stores electric energy. It's made up of 2 conducting plates separated by insulator.



P is +ve (needs e^-) and is connected to B.
B can't always be neutral so it loses part of its e^- and gives them to plate P in such a way to reach equilibrium

$$\Rightarrow U_{PB} = 0$$

When plate B becomes positive A becomes -vely charged due to accepting e^- from plate P

Notes

Charge of capacitor

$$Q = Q_B = -Q_A$$

$$Q = C \cdot U_{CA}$$

if I connect capacitor to device it acts as if generator

Quantity of Stored Energy

$$\begin{aligned} W &= \frac{1}{2} C U^2 \\ &= \frac{1}{2} \frac{Q^2}{C} \\ &= \frac{1}{2} Q \cdot U \end{aligned}$$

Notes

$$q = ne \rightarrow 1.6 \times 10^{-19}$$

$$q = It \quad \text{if current } I,$$

$$i = \frac{dq}{dt}$$

$$i = C \frac{du}{dt}$$

Use graph to Determine τ (time ct)

Tangent Passing Through Origin

$$y = At$$

slope = derivative of function

Given: $i = I(1 - e^{-\frac{t}{\tau}})$

$$\frac{di}{dt} = \frac{I}{\tau} e^{-\frac{t}{\tau}}$$

$$\text{at } t=0 \quad \frac{di}{dt} = \frac{I}{\tau}$$

Substitute $M(x, I)$ in $y = \frac{I}{\tau} t$

$$I = \frac{I}{\tau} \tau x$$


$$\frac{x}{\tau} = 1 \Rightarrow x = \tau$$

$$x = OM = \tau$$



Notes

$$\cos' = -\sin$$

$$\sin' = \cos$$

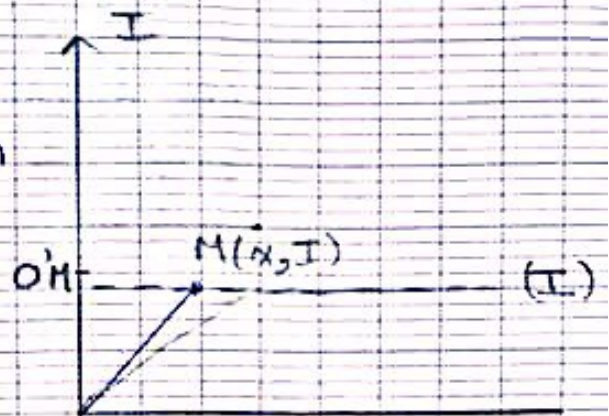

Discharging

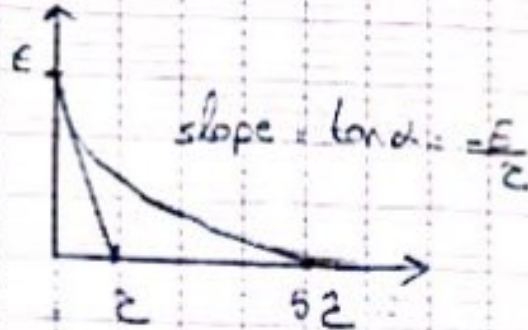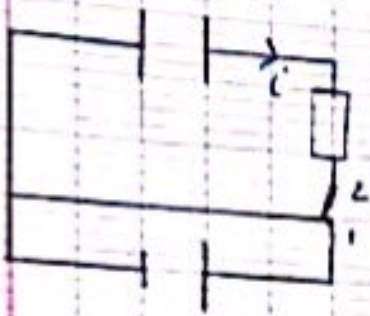

current opp direction as before (charging)

Diff eq

$$iR = u_c, \text{ but } i = -c \frac{du}{dt}$$

$$u = -RC \frac{du}{dt}$$

$$u + RC \frac{du}{dt} = 0$$

Solution

$$u = E e^{-\frac{t}{\tau}}$$

$$\text{at } t = \tau \Rightarrow u = 37\% E$$

$$q = 37\% Q$$

$$\text{at } t = 5\tau \Rightarrow u = 0.007 \approx 0$$

$$q = 0$$

Note

$$i = -I_0 e^{-\frac{t}{\tau}}$$

Note

at the end of charging or Discharging the current in capacitor is zero ($i=0$)

Alternating Sinusoidal Current

$$i = I_m \sin(\omega t + \phi)$$

↓ ↓ ↓ ↓
inst intensity max intensity angular freq phase at $t=0$

$$u = U_m \sin(\omega t + \phi)$$

inst voltage ↓ ↓ ↓ ↓
max voltage equal angular freq phase at $t=0$ (not necessarily equal)

effective current

$$I = \frac{I_m}{\sqrt{2}}$$

effective voltage

$$U = \frac{U_m}{\sqrt{2}}$$

Notes : Rules

Resistor : $u = iR$

Coil (r, L) : $u = ir + L \frac{di}{dt}$

Capacitor : $i = \frac{dq}{dt} = c \frac{du}{dt}$

Pure Resistor R

$i = I_m \sin \omega t$ reference

$\Rightarrow u = U_m \sin (\omega t + \varphi)$

- $U_m = RI_m$, $U = RI$

$\varphi = 0 \Rightarrow i$ in phase with u

Coil ($L, 0$)

$i = I_m \sin (\omega t)$

$\Rightarrow u = U_m \sin (\omega t + \varphi)$

$U_m = I_m L \omega$, $U = I L \omega$

$\varphi = \frac{\pi}{2} \Rightarrow u$ leads i by $\frac{\pi}{2}$

Capacitor C

$i = I_m \sin \omega t$

$\Rightarrow u = U_m \sin (\omega t + \varphi)$

$U_m = \frac{I_m}{C \omega}$, $U = \frac{I}{C \omega}$

$\varphi = -\frac{\pi}{2} \Rightarrow u$ lags i by $\frac{\pi}{2}$

Rule of Calculation

$$\dot{i} = c \frac{du}{dt}$$

$$du = \frac{\dot{i}}{c} dt$$

$$\int du = \int \frac{\dot{i}}{c} dt$$

$$u = \int \frac{I_m \sin(\omega t)}{c} dt$$

$$u = \frac{I_m}{c\omega} (-\cos \omega t) + k \quad \text{at } t=0 \quad k=0$$

$$u = -\frac{I_m}{c\omega} \cos \omega t$$

$$u = -\frac{I_m}{c\omega} \sin\left(\frac{\hat{\phi}}{2} - \omega t\right)$$

$$u = \frac{I_m}{c\omega} \sin\left(\omega t - \frac{\hat{\phi}}{2}\right)$$

$$u_m \sin(\omega t + \phi) = \frac{I_m}{c\omega} \sin\left(\omega t - \frac{\hat{\phi}}{2}\right)$$

$$u_m = \frac{I_m}{c\omega}, \quad \phi = -\frac{\hat{\phi}}{2}$$

$$\Rightarrow u \text{ lags } i \text{ by } \frac{\hat{\phi}}{2}$$

Note from Exercise

$$u_A = 2.4 \sin(400\hat{t} + 0.4\hat{t})$$

u capacitor loop? by $\frac{\hat{U}}{2}$

R is image of \hat{c}

$$\Rightarrow u_C = \frac{I_m}{C\omega} \sin(\omega t + 0.4\hat{t} - \frac{\hat{t}}{2})$$

Powers (Average)

$$P_{\text{resistor}} = P_{\text{generator}} = RI^2$$

in AC voltage?

$$P_{\text{av}} = UI \cos \phi$$

Capacitor $I_{\hat{c}} = \frac{\hat{U}}{Z}$

$$P = 0$$

Coil of $r=0$ $I_{\hat{L}} = \frac{\hat{U}}{Z}$

$$P = 0$$


Note

in (R-L-C)

proper freq $f_0 = \frac{1}{2\pi\sqrt{LC}}$

Note

$$f = \frac{2\pi d}{D}$$

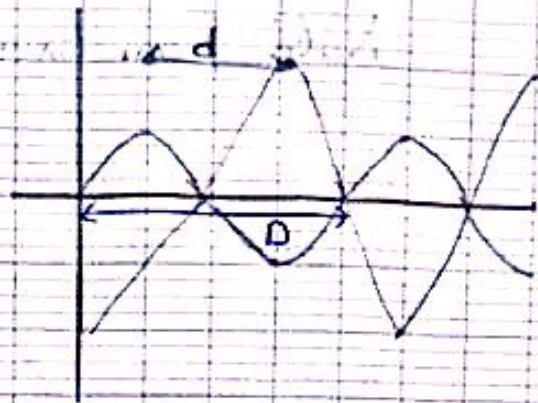


$$\begin{cases} D = 2\pi \\ d = f \end{cases} \Rightarrow f = \frac{2\pi d}{D}$$

Note

$$L\omega > \frac{1}{C\omega}$$

$$L\omega = \frac{1}{C\omega}$$

$$\frac{1}{C\omega} > L\omega$$

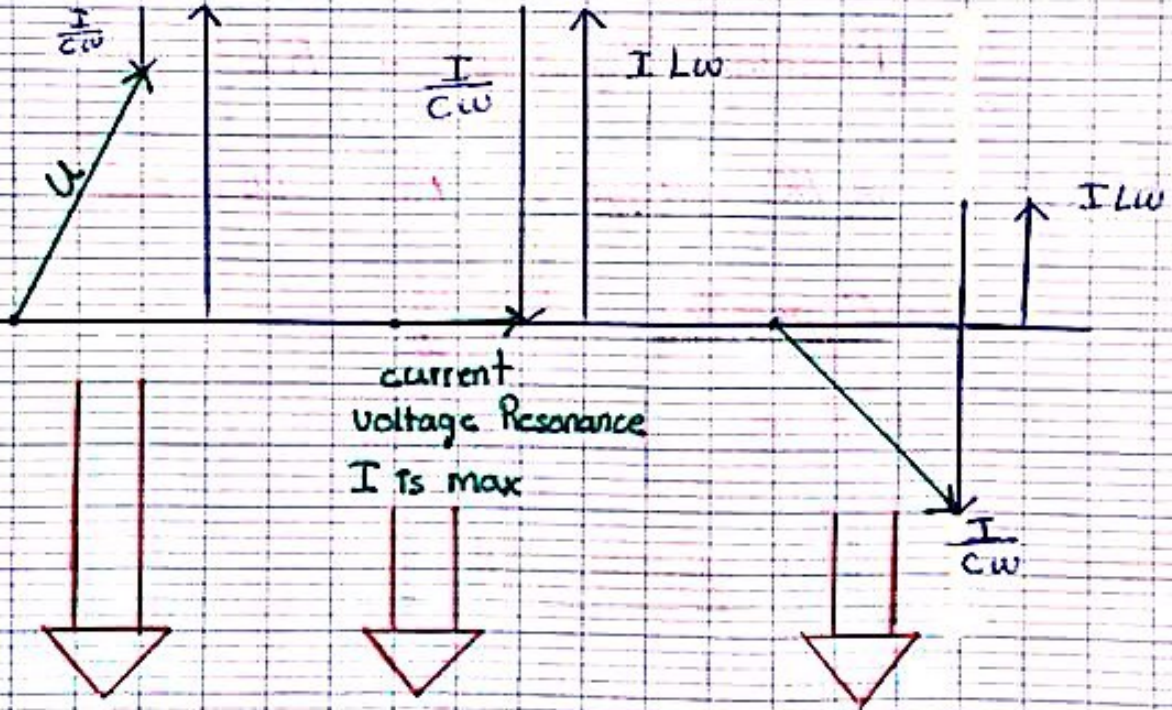

u leads i

Resonance
 \Rightarrow in phase

u lags i

Note

from Degree to rd

$$180 \longrightarrow 3.14 \text{ rd}$$

$$33.7 \longrightarrow x$$

$$\omega = 2\pi f$$